



SHANGHAI JIAO TONG  
UNIVERSITY

SCHOOL OF ELECTRONIC INFORMATION AND ELECTRICAL ENGINEERING

# A new combinational logic minimization technique

Zhaole Li

Workshop of AES, 2022



Section 1

## Introduction



The meaningful metrics for constructing optimal combinational circuits are gate count, depth, energy consumption, etc.

The number of  $n$ -variable Boolean functions is  $2^{2^n}$ , so no known techniques can even find the optimal circuits for 8-variable Boolean functions. Thus we build the implementations using some heuristics.



- ① This work presented a new technique for circuit implementations with two steps:
  - ① Reducing multiplicative complexity for the non-linear components;
  - ② Then optimizing the linear components.
- ② The metric is gate count with AND, XOR and 1;

## Definition

The multiplicative complexity of a function is the number of  $\mathbb{F}_2$  multiplications necessary and sufficient to compute it.

## Example

The multiplicative complexity of  $f(x_1, x_2, x_3, x_4) = x_1x_2x_3x_4 + x_1x_2x_3 + x_1x_2x_4 + x_2x_3x_4 + x_1x_2 + x_1x_3 + x_1x_4 + x_2x_3 + x_3x_4$  is no greater than 3 since  $f = (x_1 + 1)(x_2 + 1)(x_3 + 1)(x_4 + 1) + x_1 + x_2 + x_3 + x_4 + 1$  and is 3 due to  $\deg(f) = 4$ .



The second step is composed by finding the maximal linear components of the circuit and minimizing the number of XOR gates needed. A new heuristic for the second step is proposed.

## Non-linear components of Sbox in AES<sup>1</sup>

---

<sup>1</sup>Boyar J, Peralta R. A new combinational logic minimization technique with applications to cryptology[C]//International Symposium on Experimental Algorithms. Springer, Berlin, Heidelberg, 2010: 178-189.

The only non-linear component in AES's Sbox is to compute the inverse in the finite field  $\mathbb{F}_{2^8}$ . Canright built a circuit for inverses in  $\mathbb{F}_{2^8}$  by giving a circuit for inverses in  $\mathbb{F}_{2^4}$ . Using the same general technique but in different bases<sup>2</sup>  $\{W, W^2, Z^2, Z^8\}$  we can represent an element  $\Delta = (x_0W + x_1W^2) Z^2 + (x_2W + x_3W^2) Z^8$  of  $\mathbb{F}_{2^4}$ , and the inverse of this element  $\Delta' = (y_0W + y_1W^2) Z^2 + (y_2W + y_3W^2) Z^8$  can be calculated as the following:

---

<sup>2</sup> $W$  is a root of  $x^2 + x + 1$  over  $\mathbb{F}_2$ ,  $Z$  is a root of  $x^2 + x + W$  over  $\mathbb{F}_{2^2}$ .



$$\begin{cases} -y_0 = x_1x_2x_3 + x_0x_2 + x_1x_2 + x_2 + x_3 \\ -y_1 = x_0x_2x_3 + x_0x_2 + x_1x_2 + x_1x_3 + x_3 \\ -y_2 = x_1x_0x_3 + x_0x_2 + x_0x_3 + x_0 + x_1 \\ -y_3 = x_1x_2x_0 + x_0x_2 + x_0x_3 + x_1x_3 + x_1 \end{cases}$$



For  $\mathbb{F}_{2^4}$  inversion, we take the method:

- ① pick an equation and build an efficient circuit for it;
- ② store the intermediate functions used in above for possible usage in the other equations;
- ③ iterate until all equations have been computed.

## Remark:

It turns out that 3 multiplications are enough to compute any functions on four variables.



$$\begin{cases} -y_1 = (x_0x_2 + x_1)(x_2 + x_3) + x_3 \\ -y_3 = (x_0x_2 + x_3)(x_0 + x_1) + x_1 \\ -y_0 = (x_0x_2 + y_1)x_3 + y_1 + x_2 + x_3 \\ -y_2 = (x_0x_2 + y_3)x_3 + y_3 + x_0 + x_1 \end{cases}$$

This circuit needs 5 AND gates and 11 XOR gates.

## Section 3

# Minimizing linear components<sup>3</sup>

---

<sup>3</sup>Boyar J, Peralta R. A new combinational logic minimization technique with applications to cryptology[C]//International Symposium on Experimental Algorithms. Springer, Berlin, Heidelberg, 2010: 178-189.

## Example

$$\begin{pmatrix} 1 & 1 & 0 & 0 \\ 1 & 1 & 1 & 0 \\ 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 1 \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \\ x_3 \\ x_4 \end{pmatrix}$$

Actually written in the equations  $x_1 + x_2; x_1 + x_2 + x_3; x_1 + x_2 + x_3 + x_4; x_2 + x_3 + x_4$ .  
It's easy to see that we only need 4 XOR to compute the linear component  
 $v_1 = x_1 + x_2; v_2 = v_1 + x_3; v_3 = v_2 + x_4; v_4 = v_3 + x_1$ .

Let  $S$  be a set of linear functions. For any linear predicate  $f$ , we define the distance  $\delta(S, f)$  as the minimum number of additions of elements from  $S$  necessary to obtain  $f$ . For the linear Boolean function, initially  $S$  is just the set of all variables  $x_1, x_2, \dots, x_n$ , then a new base element is the form of two old base elements, update the  $\delta(S, f)$  until  $\delta(S, f) = 0$ .

- ① For the  $(n, m)$ -linear Boolean functions, we use the  $m \times n$  matrix over  $\mathbb{F}_2$  such as  $f(\mathbf{x}) = M\mathbf{x}$ .  $S$  still be just the set of all variables  $x_1, x_2, \dots, x_n$ ;
- ② Denote  $Dist[]$  the distance from  $S$  to the linear function given by rows of  $M$ , in fact,  $Dist[i] = \delta(S, f_i)$  where  $f_i$  is the  $i^{th}$  linear function given by  $M$ ;
- ③ Pick a new base element by adding two old base elements and then update  $Dist[]$ ;
- ④ Iterate the last step until  $Dist[] = (0, 0, \dots, 0)$ .



- ① pick those that minimize the sum of new distances;
- ② pick one that maximizing the Euclidean norm of the vector of new distances;

This criterion seems strange for maximizing. But we want a distance  $(0, 2, 1)$  rather than  $(1, 1, 1)$ .

We build the circuit of the following equation system:

$$y_0 = x_0 + x_1 + x_2$$

$$y_1 = x_1 + x_3 + x_4$$

$$y_2 = x_0 + x_2 + x_3 + x_4$$

$$y_3 = x_1 + x_2 + x_3$$

$$y_4 = x_0 + x_1 + x_3$$

$$y_5 = x_1 + x_2 + x_3 + x_4$$

so the matrix  $M$  is 
$$\begin{pmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 1 \\ 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 1 & 1 & 0 \\ 1 & 1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 1 & 1 \end{pmatrix}.$$



- ① In above situation, the initial  $S$  is the set  
 $\{[00001], [00010], [00100], [01000], [10000]\}$ ;
- ② The initial distance is  $Dist = [2, 2, 3, 2, 2, 3]$ ;
- ③ First choose the two coloumn which have the most 1 in the same row;
- ④ ...



SHANGHAI JIAO TONG  
UNIVERSITY

Thank You

Zhaole Li · A new combinational logic  
minimization technique